

# **CSE 260M / ESE 260**

# **Intro. To Digital Logic & Computer Design**

Bill Siever  
&  
Michael Hall

# This week


- Thursday: Studio — Need 1 Hw kit and cable for each group!
- Exam 1: Will be returned later this week
  - Midterm Grades on Canvas, etc. soon after
- Hw 4A probably returned too
- Hw 4B posted tonight:
  - Due Monday, March 18th @ 11:59pm (reading for ch 5 also due then!)

# Chapter 4

# Review: HDLs *Describe* Hardware


- Uses
  - Simulation: Confirm modules work together
  - “Synthesis” : Transformation to real hardware
    - Like compilers used for programming languages
- Use *modules* for hierarchical design — important part of managing complexity
- Description Styles
  - Structure (connect 2 input AND to ...)
  - Behavior (if x then y)

# (System) Verilog Module: Review

 


```
module example(input logic a, b, c,  
               output logic y);  
    // module body goes here  
endmodule
```

 Input & Output  
are like the Pins  
On chips or in  
JLS


 
# (System) Verilog

- Conditionals via Ternary operator (? :)



```
module mux2(input logic [3:0] d0, d1,  
            input logic s,  
            output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```


Behavioral

# 8-bit mux2: Hierarchical

```
module mux2_8(input logic [7:0] d0, d1,  
             input logic s,  
             output logic [7:0] y);
```

```
    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);  
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);
```

```
endmodule
```

 

# Sequential Logic




# always: Based on *Events*

- Concept of “event” is related to simulation and “event driven programming”
- JLS uses events: An OR gate “reacts” to events and schedules an update  
See [here](#)
 
# Discrete Time Event Simulator

- Computes all activities / updates for “now”
  - They cause new activities that need to be handled in the future (at:  $\text{now} + \text{prop delay}$ ). Those are put in a queue at for that time.  
Ex: Update an or-gate’s output at  $\text{now}+4$
- Move on to “now +1”, repeat



# Discrete Time Event Simulator

- Updating values in current turn: Incrementally or all at once at end of turn
  - Ex: Assume x is 1 and y is 0
  - Incremental:
    - $x = 0$
    - $y = x$
  - x's final value is 0  
y's final value is 0 too
- All at once / end of turn
  - $x \leq 0$
  - $y \leq x$
- x's final value is 0  
y's final value is 1

# SystemVerilog Standard

- Why all the simulation details?
- Quick intro to SystemVerilog Standard
  - Section 9 / 9.2

# always Statement

- Form:

```
always @(sensitivity list)  
    statement;
```

- When event in sensitivity list occurs, statement is executed
- Ex: 

```
always @(posedge clock)  
    statement;
```
- Verilog: Don't use this in here

# always Statement

- Form:

```
always @(sensitivity list)  
statement;
```

- When event in sensitivity list occurs, statement is executed
- Verilog: *Don't use this in here*

# always in 260

- Form 1: Comb logic

```
always_comb  
  statement;
```

Use blocking assignment (=)

- Statement(s) are (complex) combinational logic. Like if/else or case.  
Updates when any (relevant/used) input changes

- Form 2: Registered (synchronous, synthesize able, sequential) logic

```
always_ff @(sensitivity list)  
  statement;
```

Use non-blocking assignment (<=)

- Often @(posedge clock) used

# Assignments

- **Form 1: Continuous Assignment**  
`assign var = expression;`
  - **Continuously assigned!** Largely a wired connection
- **Forms 2 & 3 in Procedures** (in some form of `always*`):
  - **Blocking (=):** Will be “instant” in terms of simulation
    - `always_comb`
  - **Non-Blocking (<=):** Will occur at end of turn all at once
    - `always_ff`




# Rules for Assignments

- **Synchronous sequential logic**  
use `always_ff @(posedge clk)` and nonblocking assignments (`<=`)  

```
always_ff @(posedge clk)
    q <= d; // nonblocking
```
- **Simple combinational logic**  
use continuous assignments (`assign`)  


```
assign y = a & b;
```
- **Complex Combinational Logic**  
use `always_comb` and blocking assignments (`=`)
- **Assign signals in only one `always` or `assign` statement!**

# Verilog: D Flip-Flop

 

```
module flop(input logic clk,  
            input logic [3:0] d,  
            output logic [3:0] q);  
    always_ff @(posedge clk)  
        q <= d; // pronounced "q gets d"  
endmodule
```


# Resettable D-Flip-Flop 1

 

```
module flopr(input logic clk,
             input logic reset,
             input logic [3:0] d,
             output logic [3:0] q);

    always_ff @(posedge clk)
        if (reset) q <= 4'b0;
        else q <= d;
endmodule
```


# Resettable D-Flip-Flop 2

 

```
module flopr(input logic clk,
             input logic reset,
             input logic [3:0] d,
             output logic [3:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 4'b0;
        else      q <= d;
endmodule
```

# Resettable D-Flip-Flop 3

 

```
module flopr(input logic clk,
            input logic reset,
            input logic en,
            input logic [3:0] d,
            output logic [3:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 4'b0;
        else if (en) q <= d;
endmodule
```

# always and Combinational Logic

```
always_comb  
begin  
    y = a & b  
    ...  
end
```

Block of assignments

Could have been done with individual assigns

Notice = ("blocking assignment"), not <= ("non-blocking assignment")


# always\_comb has nice features

- case : Selection between several options  
Great for state machines!
- Must describe all possible combinations to be comb logic. Use default

```
case (state)
  soap:                hot = 1;
  highPressureWarm:   hot = 1;
  ...
  default: hot = 0;
endcase
```

 
# Verilog FSMs

- Three parts
  - Next state logic (arrows / next state table)
  - State register (active bubble)
  - Output logic (output equations)







# Divide by 3 Counter

 
 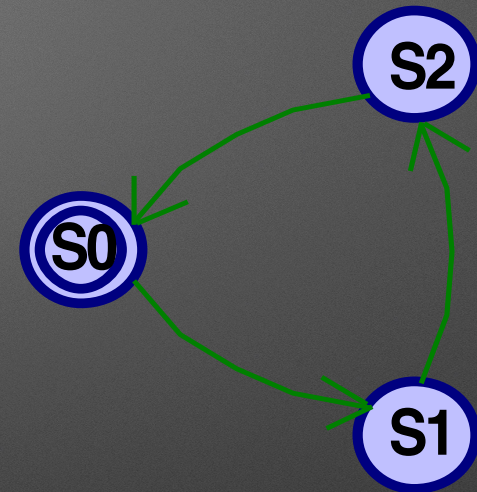
# Verilog

```
module divideby3FSM(input  logic clk,  
                   input  logic reset,  
                   output logic q);  
  
    typedef enum logic [1:0] {S0, S1, S2} statetype;  
    statetype state, nextstate;  
  
    // state register  
    always_ff @(posedge clk, posedge reset)  
        if (~reset) state <= S0;  
        else      state <= nextstate;  
  
    // next state logic  
    always_comb  
        case (state)  
            S0: nextstate = S1;  
            S1: nextstate = S2;  
            S2: nextstate = S0;  
            default: nextstate = S0;  
        endcase  
  
    // output logic  
    assign q = (state == S0);  
endmodule
```



# Parameterized Modules: Declaration

- Way to specify additional details for an *instance* of a generic part
  - Commonly the “width” of the part

```
module mux2
  #(parameter width = 8) // name and default value
  (input  logic [width-1:0] d0, d1,
   input  logic           s,
   output logic [width-1:0] y);
  assign y = s ? d1 : d0;
endmodule
```

# Parameterized Modules: Use

- Default or specify parameter for instance:

```
mux2 myMux(d0, d1, s, out);
```

```
mux2 #(12) lowmux(d0, d1, s, out);
```

# Ports: Positional vs. Named

- Default or specify parameter for instance:

```
logic a, b, sel, y
mux2 myMux(a, b, sel, y);
```

vs.

```
mux2 myMux(.d0(a), .d1(b),
           .s(sel), .out(y));
```

```
module mux2
    #(parameter width = 8)
    (input logic [width-1:0] d0,
     input logic [width-1:0] d1,
     input logic s,
     output logic [width-1:0] y)
    assign y = s ? d1 : d0;
endmodule
```

# **Test Bench: Overview & Concept (Simple w/ Asserts)**

# Hw4A: simple\_comb\_tb

# FPGA: Field Programmable Gate Array



# FPGA


- Field Programmable
- Gate Array
  - Lattice iCE40 UP5k: Architecture Overview
    - RAMs, (Dual and Single Port)
    - Look Up Tables (LUTs): 4 inputs
    - D Flip Flops
    - Lots: ~5,000

**Playground: Combinational logic,  
hardware, synthesis, and parameters**

# Questions

# Adders

**Half Adder**

 


A	B	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

**Full Adder**

 

$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

# Ripple Carry Adder: Propagation Delay

